

Electricity and Water

The Water Pump

1. [4-2/1/1]

Electrons flow from the _____ to the _____ side of a battery.

- A. negative, positive
- B. positive, negative
- C. positive, neutral

2. [4-2/1/2]

Electricity involves many terms that can be directly related to water or plumbing. Voltage is comparable to, and can be thought of as, the _____ that pushes water through pipes. Current is the amount of _____ actually flowing through the pipes at any given time.

- A. temperature, water
- B. pressure, pressure
- C. pressure, water

3. [4-2/1/2]

The greater the _____ (voltage) in a line, the greater the amount of _____ (electric current) that flows.

- A. water pressure, water
- B. back flow, air
- C. restriction, molecules

4. [4-2/2/2]

Using the water analogy, the alternator can be thought of as the _____ which provides water pressure to the _____ and the _____.


- A. battery, electrical ground, propeller
- B. pump, primary bus, avionics bus
- C. pump, radio, fuel tank

5. [4-2/2/5]

A spinning alternator causes electric _____ to flow into the primary bus and through the electrical equipment. It then returns to its _____ source in a manner similar to the tray in our water analogy. This tray is called the _____.

- A. current, original, electrical ground
- B. force, battery, oil pan
- C. pressure, alternator, battery

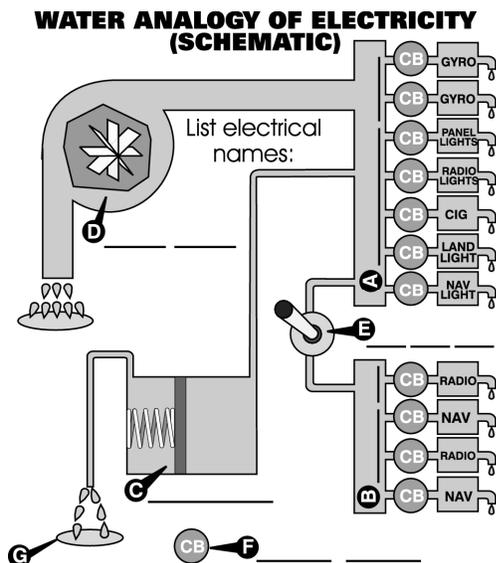6. [3-3/Figure 5] Label the individual components of the water analogy circuitry:





Rod Machado's Sport Pilot Workbook

The Electrical Ground

7. [4-3/3/2]

The electrical ground is not the ground upon which you stand. It's usually the airplane's _____.

- A. battery
- B. metal frame
- C. ground wire

Load Meter

8. [4-4/1/2]

A load meter is located between the _____ and the _____ of our water (electrical) system.

- A. pump (alternator), starter
- B. pump (alternator), battery
- C. pump (alternator), primary bus

9. [4-4/1/2]

The load meter shows the _____ placed on the pump (alternator) by the airplane's water (electrical) system.

- A. pressure (voltage)
- B. water load (current)
- C. resistance

10. [4-4/1/3]


A zero reading on the load meter (a full left deflection) means that the water pump (alternator) _____ providing pressure to the primary bus.

- A. is
- B. isn't
- C. Both of the above.

11. [4-4/Figure 7]

Based on the water analogy circuit below, the load meter would be located at _____.

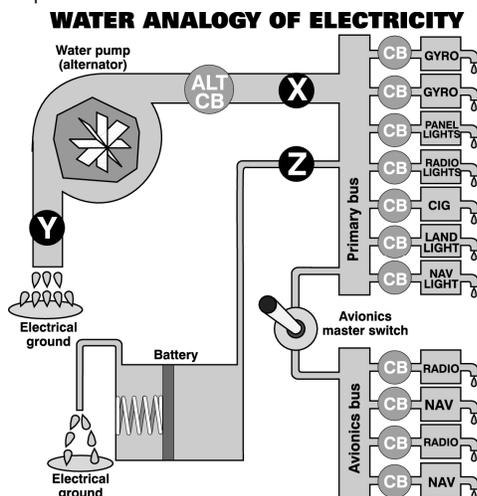- A. position Z
- B. position X
- C. position Y



12. [4-4/1/3]

A zero reading on the load meter means the alternator _____ providing electricity to the primary bus or there is _____ electrical current drawn by the airplane's electrical equipment. This can happen when the _____ fails or all the airplane's electrical equipment is turned off.

- A. isn't, no, alternator
- B. is, little, battery
- C. isn't, no, ground wire

13. [4-4/3/1]

Amps are a measure of _____ flow.

- A. voltage
- B. current
- C. water pressure

14. [4-4/3/2]

Circuit breakers protect electrical equipment and wires from receiving more _____ than they can safely handle.

- A. current
- B. voltage
- C. resistance

The Battery

15. [4-5/2/2]

In the actual electrical system, the battery _____ stores the electrical charge provided by the alternator.

- A. spring
- B. mechanically
- C. chemically

16. [4-5/2/2]

It's the _____ which allows you to operate the airplane's electrical equipment when the engine isn't running or when the alternator fails in flight.

- A. alternator
- B. propeller
- C. battery

Battery Potential

17. [4-5/3/2]

A 35 amp hour battery should (in theory) provide _____ amps of continuous current to the electrical system for one hour.

- A. 35
- B. 17.5
- C. 3.5

Chapter 4 - Electrical Systems: Knowing What's Watt

18. [4-5/3/4]

While airplane batteries are rated at 12 or 24 volts, airplane electrical systems (their alternators) are rated for ____ or ____ volts.

- A. 12, 24
- B. 14, 28
- C. 7, 14

The Charge-Discharge Ammeter

19. [4-6/1/1]

Between the positive terminal of the battery and the primary bus is an ammeter, called a ____ ammeter.

- A. charge-discharge
- B. battery
- C. load

20. [4-6/1/1]

As the name implies, the charge-discharge ammeter tells you if electrical current is flowing into or out of the ____.

- A. load meter
- B. alternator
- C. battery

21. [4-6/1/2]

A positive deflection of the charge-discharge ammeter usually implies that the battery is being ____.

- A. charged
- B. discharged
- C. neutralized

22. [4-6/1/2]

A negative needle deflection on the charge-discharge ammeter usually implies that the ____ is supplying the primary bus with electrical current.


- A. ammeter
- B. regulator
- C. battery

23. [4-6/Figure 12]

Based on the water analogy circuit to the top right, the charge-discharge ammeter would be located at ____.

- A. position Y
- B. position X
- C. position Z

WATER ANALOGY OF ELECTRICITY

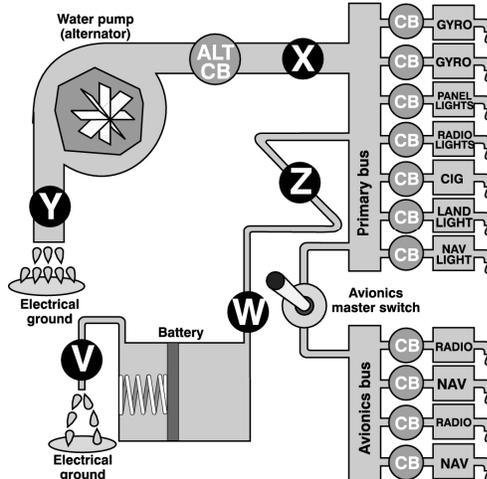

24. [4-6/1/3]

Normally, the needle of the charge-discharge ammeter should be resting near the ____ or ____ mark. This implies that the battery is neither being charged nor discharged (a good sign).

- A. zero, center
- B. full left, full right
- C. 0, 60

25. [4-6/2/2]

After startup, the battery is sure to be slightly drained. You can expect to see a ____ needle deflection of five, maybe six or seven needle widths on the ammeter right after engine start.

- A. positive (+)
- B. neutral (+/-)
- C. negative (-)

26. [4-7/1/2]

Most airplane operation manuals suggest that after approximately ____ of cruising flight, the ammeter needle should return to within a two-needle-width deflection from center on the positive (+) or charging side.


- A. 1 minute
- B. 10 minutes
- C. 30 minutes

Rod Machado's Sport Pilot Workbook

27. [4-6/Figure 14 & 4-7/Figure 15]

Based on the schematic below, which ammeter (Y or Z) goes with which circuit (W or X)?

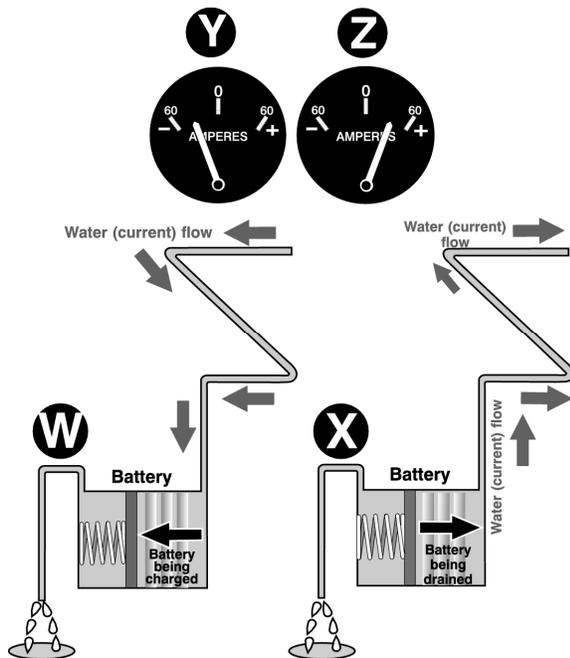- A. Y goes with circuit W, Z goes with circuit X.
- B. Y goes with circuit X, Z goes with circuit W.
- C. Y goes with circuit W, Z goes with circuit W.



28. [4-7/1/2]

Excess voltage resulting from a battery overcharge can ____ battery fluid (electrolyte), damaging the battery and possibly causing a battery ____.

- A. replenish, freeze
- B. boil off, fire
- C. boil off, charge

29. [4-7/1/3]

A needle deflection on the ____ side means current is flowing out of the battery onto the primary bus

- A. 0 or 60
- B. positive (+)
- C. negative (-)

Load Meters

30. [4-7/3/3]

Load meters provide important indications about the health of the airplane's electrical system. Unlike charge-discharge ammeters, they are calibrated to reflect the actual ____ load placed on the alternator.

- A. ampere
- B. voltage
- C. resistance

31. [4-8/1/1]

Load meters with a zero or full-left deflection indicate the alternator ____ providing current to the primary bus.

- A. is
- B. isn't
- C. should be

32. [4-8/1/1]

During flight with electrical equipment in use, a full left deflection of the load meter needle is similar to a charge-discharge ammeter reading pointing to the ____ side of its scale.

- A. negative (-)
- B. neutral
- C. positive (+)

33. [4-8/1/2]

A load meter needle deflection to the right of the zero index represents the ____ drain on the alternator.


- A. electrical voltage
- B. electrical current
- C. electrical resistance

34. [4-8/1/2]

If you add all the electrical current used by the active electrical equipment, this sum should be equal to the amount of the load meter ____ deflection.

- A. needle's
- B. voltage
- C. negative

35. [4-8/Figure 17]

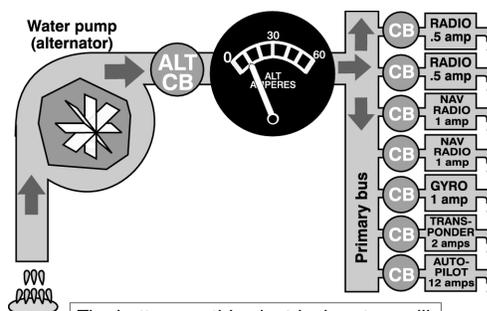


The battery on this electrical system will:

- A. overcharge.
- B. undercharge.
- C. remain unaffected.

Chapter 4 - Electrical Systems: Knowing What's Watt

36. [4-8/Figure 18]

The Voltage Regulator

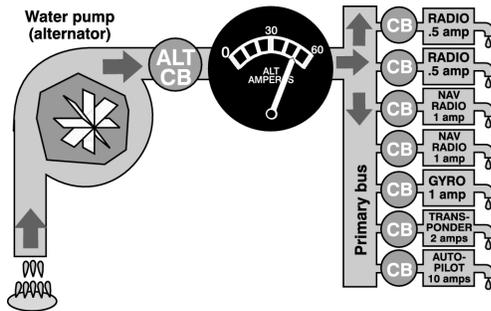

The battery on this electrical system will:
 A. overcharge.
 B. undercharge.
 C. remain unaffected.

Electrical Drain

37. [4-8/1/4]

Radios typically consume _____ amp(s) of current while receiving and about _____ amps(s) while transmitting.

- A. one-half, 5
- B. 5, one-half
- C. 1, 2

38. [4-8/2/2]

With two radios, two nav radios, one electric gyro, a transponder and an autopilot in use, a 16 amp deflection should be shown on the load meter. A needle deflection less than 16 amps implies that the _____ isn't providing enough current to run the equipment.

- A. resistor
- B. battery
- C. alternator

39. [4-8/3/1]

Load meter needle deflections less than the summed amperage of active and properly working electrical equipment imply that the _____ will eventually be _____.

- A. alternator, drained
- B. battery, drained
- C. electrical ground, shorted

40. [4-8/3/2]

Suppose the load meter's needle deflection is greater than the needs of the electrical equipment. This can lead to

- A. engine failure.
- B. pilot failure.
- C. evaporating battery fluid or battery and electrical fires.

41. [4-9/3/1]

Voltage regulators or alternator control units (they're essentially the same thing) regulate the _____ output.

- A. engine's
- B. alternator's
- C. battery's

42. [4-9/3/1]

Voltage regulators help alternators maintain a _____ voltage output under varying RPM conditions.

- A. constant
- B. low
- C. high

43. [4-10/1/1]

Alternators need a little bit of electricity running through them before they'll start producing electricity. This small amount of electrical prime is called the _____.

- A. battery field current
- B. primary bus current
- C. alternator field current

Problems With Brains

44. [4-11/1/2]

If your airplane has a low-voltage light, it can illuminate

- A. during low engine idle.
- B. when the alternator has been taken offline.
- C. Both of the above.

45. [4-11/1/4]

If your airplane has a high-voltage warning light, it can activate:

- A. when the alternator puts out excessive voltage.
- B. if the voltage regulator malfunctions.
- C. Both of the above.

46. [4-11/1/5]

If you need the equipment that was disabled by a popped circuit breaker, a good recommendation is to never reset the circuit breaker _____.

- A. more than two times
- B. more than one time
- C. at all



Rod Machado's Sport Pilot Workbook

47. [4-D11/2/1]

Manually taking the alternator offline becomes an important consideration if _____ condition occurs and the circuitry doesn't _____ isolate the alternator.

- A. a battery full, fully
- B. an overvoltage, automatically
- C. an isolated voltage, reset and

Making Connections

48. [4-D12/1/3]

If the battery is dead, the _____ isn't going to work.

- A. magneto
- B. engine
- C. alternator

49. [4-D12/1/5]

If the voltage regulator goes bad and the alternator produces too much voltage, you can take the alternator offline by pulling the _____ circuit breaker.

- A. main alternator
- B. battery terminals off the
- C. avionics

50. [4-D12/1/5]

Turning off the alternator half of the master switch on many airplanes will shut off the _____ field current flow, thus deactivating the _____.

- A. alternator, alternator
- B. engine's, battery
- C. alternator, engine

51. [4-D13/1/2]

If faced with an errant voltage regulator in flight which forces you to deactivate the alternator, unload the system by turning off _____ equipment.

- A. all essential electrical
- B. all mechanical
- C. all nonessential electrical

52. [4-14/Figure 25 & D15/Figure 27]

Compare the water analogy circuitry with the airplane's electrical circuit below.

52. [D14/Figure 25 & D15/Figure 27]


Compare the water analogy circuitry with the airplane's electrical circuit below.



Chapter 4 - Electrical Systems: Knowing What's Watt

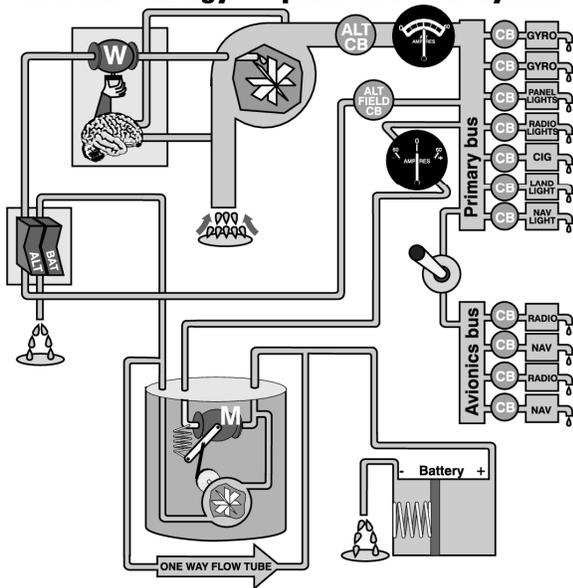1. A
2. C
3. A
4. B
5. A
6. A/primary buss, B/avionics bus, C/battery, D/alternator, E/avionics master switch, F/circuit breaker, G/electrical ground
7. B
8. C
9. B
10. B
11. B
12. A
13. B
14. A
15. C
16. C
17. A
18. B
19. A
20. C
21. A
22. C
23. C
24. A
25. A
26. C
27. B
28. B
29. C
30. A
31. B
32. A
33. B
34. A
35. B
36. A
37. A
38. C
39. B
40. C
41. B
42. A
43. C
44. C
45. C
46. B
47. B
48. C
49. A
50. A
51. C

The Water Analogy: Airplane Electrical System



MODIFIED ELECTRICAL SCHEMATIC

